
 


Logic Simulation

 
- Introduction
- Simulation Models
- Logic Simulation Techniques
- Issues of Logic Simulations
 - ♦ Hazards
 - ♦ Oscillation
- Conclusions



Quiz Review



t	L_E	L_A	Scheduled events
0	(B,1)	G_1	(E,1)@8
2			
4			
8	(E,1)	G_2, G_3	(H,1)@16; (J,0)@12
10			
12	(J,0)	G_4	(K,1)@18
14			
16	(H,1)	G_4	(K,0)@22
18	(K,1)		
22	(K,0)		

 

Hazard [Huffman 57] [McCluskey 62]

- Hazard : Output signal waveform depends on

- ♦ (Internal) circuit delay and (external) input signal change

- Two types of hazards:

- ① **Static hazard:** A momentary change of gate output that does not cause the steady gate output to change


- ♦ Static-1 hazard: steady output is 1

- ♦ Static-0 hazard: steady output is 0


- ② **Dynamic hazard:** A momentary change of gate output during rising or falling transition (no more details in this lecture)



static-1
hasard

 

static-0
hasard

 

dynamic-1
hasard




dynamic-0
hasard


Hazard also called *glitch*, *spike*

Why Hazard?

 ① **Logic hazard:** signal change reconverge with different timing




 ② **Function hazard:** more than one input changes




Logic Hazard Can be Improved by Circuit Design;
Function Hazard Cannot.

Test Timing Is Important

 

- **Strobe time** = time to observe output
- Example: expect output = 0
 - ♦ Strobe time = 16 → **pass**
 - ♦ Strobe time = 20 → **fail**
 - ♦ Strobe time = 24 → **pass**

 Need to Consider Hazards to Decide Test Timing




How to Detect Hazard?

- Event-driven simulation is too slow
- **Six-valued Logic** is used to detect potential static hazards

Value	Meaning
0	Static 0
1	Static 1
R	Rising transition, 0→1
F	Falling transition, 1→0
0*	Static-0 hazard
1*	Static-1 hazard

AND	0	1	R	F	0*	1*
0	0	0	0	0	0	0
1	0	1	R	F	0*	1*
R	0	R	R	0*	0*	R
F	0	F	0*	F	0*	F
0*	0	0*	0*	0*	0*	0*
1*	0	1*	R	F	0*	1*

 6-valued simulation cannot determine **for sure** if there is a hazard or not. It can only indicate “potential” hazards.




Quiz

Q: Please fill in 6-valued table for NOR gate
A:

NOR	0	1	R	F	0*	1*
0	1	0	F	R	1*	0*
1	0	0	0	0	0	0
R	F	0				0*
F	R	0				0*
0*	1*	0				0*
1*	0*	0	0*	0*	0*	0*



Apply 6-valued Simulation

 


AND	0	1	R	F	0*	1*
0	0	0	0	0	0	0
1	0	1	R	F	0*	1*
R	0	R	R	0*	0*	R
F	0	F	0*	F	0*	F
0*	0	0*	0*	0*	0*	0*
1*	0	1*	R	F	0*	1*

NOR	0	1	R	F	0*	1*
0	1	0	F	R	1*	0*
1	0	0	0	0	0	0
R	F	0	F	0*	F	0*
F	R	0	0*	R	R	0*
0*	1*	0	F	R	1*	0*
1*	0*	0	0*	0*	0*	0*

Quiz


Q: Please run 6-valued simulation to determine whether there is static hazard on output?

A:

 


Logic Simulation

 - Introduction
- Simulation Models
- Logic Simulation Techniques
- Issues of Logic Simulations
 - ♦ Hazards
 - ♦ Oscillation
- Conclusions




Quiz

 Q: Simulate this circuit with initial values
 $S'=1$, $R'=1$, $y=0$, $y'=1$
 Draw output waveforms.




t	L_E	L_A	Scheduled events
0	(S',0)		
4	(S',1)		

 

Oscillation

- This is RS-latch with inverted inputs
- RS-latch is oscillating

S'	R'	y	y'
0	1	1	0
1	0	0	1
1	1	Last state	Last State
0	0	forbidden	forbidden

 

Simulator Must Stop Oscillation. How?

Local Oscillation Control

- Two methods:


- 1) Monitor user-specified conditions on latches/FF

- * Example: when $y=y'=0$, **simulator forces** $y = u$, $y' = u$

- 2) Oscillation control via modeling


- * Example: when $y = y' = 0$, **$G = u$** , $y = y' = u$, **oscillation stops**

- * Example: replace it by **SR-latch**

 

Global Oscillation Control

 - Count events occurring after any primary input change
- If number of events exceeds specified limit
 - ♦ Stop simulation and report warning
- Global feedback loop also cause fault sim./test gen. problem
 - ♦ see fault simulation 5.7



Global Feedback Should be Avoided


Conclusions

- Types of Hazards
 - ♦ Static-0 hazard, static-1 hazard
 - ♦ Dynamic-0 hazard, dynamic-1 hazard
- Why hazard?
 - ♦ Logic hazard: signal reconverges with differing timing
 - ♦ Function hazard: multiple input change
- 6-valued simulation can detect potential hazard
 - ♦ without event-driven simulation
- Oscillation should be suppressed by simulator
 - ♦ Local/Global oscillation control


Logic Sim. is Building Block for Many EDA Tools

FFT

- Q: what would happen in real circuits?

 

S'	R'	y	y'
0	1	1	0
1	0	0	1
1	1	Last state	Last State
0	0	forbidden	forbidden

 

References

- **[Huffman 1957] D. A. Huffman, “Design and Use of Hazard-free Switching Networks,” J. ACM 4, pp.47, 1957.**
- **[McCluskey 1962] E.J. McCluskey, “Transients in Combinational Logic Circuits,” Redundancy Techniques for Computing Systems, pp.9-46, Spartan Book, 1962.**
- **[Ulrich 1965] Ulrich, “Time sequenced logical simulation based on circuit delay and selective tracing of active network paths”, ACM Nat’l Conference, pp.437-448, 1965.**