

BIST Part 2

- Output Response Analysis

- ◆ Simple ORA

- ◆ LFSR-based ORA

- * Serial : compress one bit at a time

- CRC Theory

- PAL analysis


- How to design LFSR as ORA?

- * Parallel : compress multiple bits at a time

- BIST Architecture


- Issues with BIST

- Conclusions

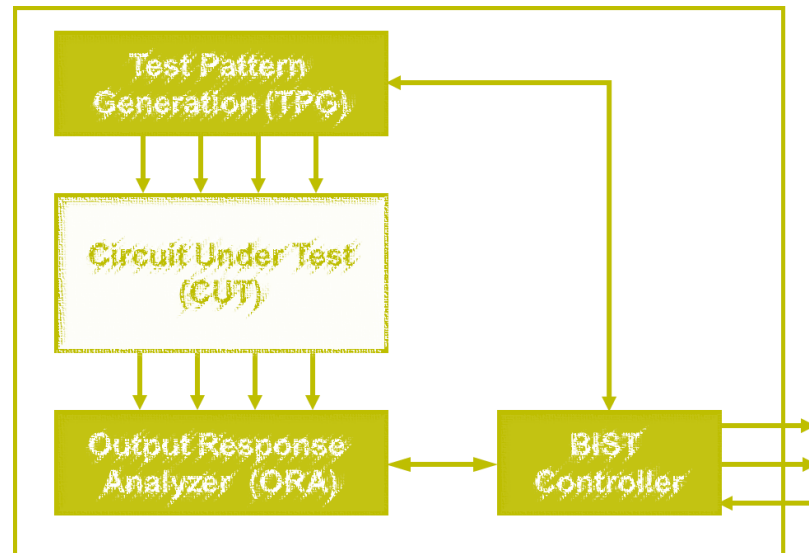


LFSR (Review)

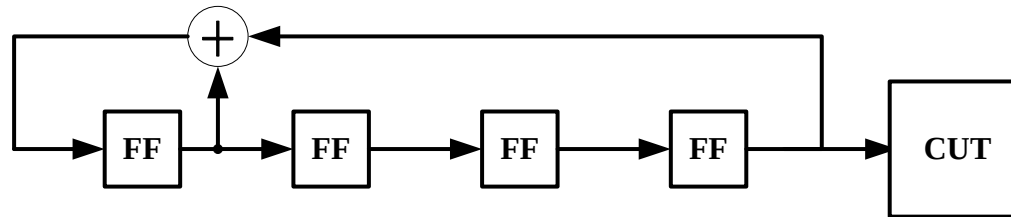
- LFSR consist of **FF** and feedback **XOR**
- Two applications of LFSR:
 - ♦ 1. LFSR without external input
 - * Used for **TPG**



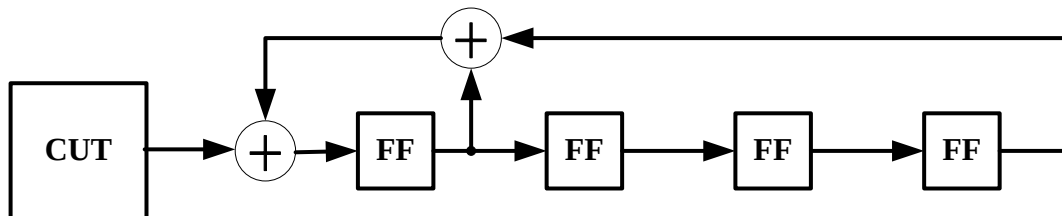- ♦ 2. LFSR with external input
 - * Used for **ORA**



LFSR as ORA

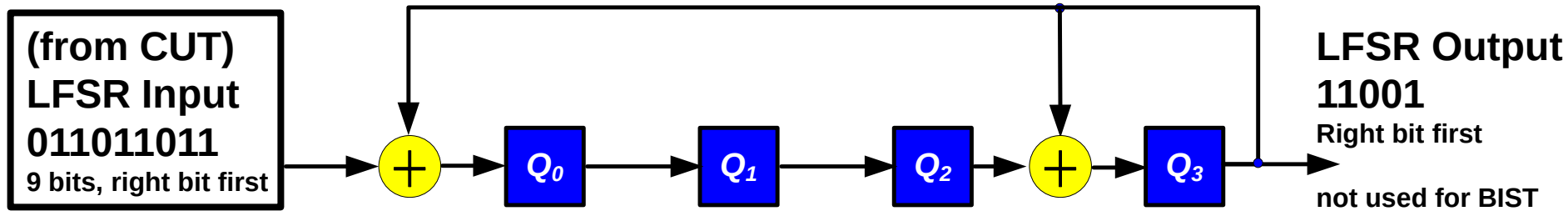

cycle	LFSR input	Q ₀	Q ₁	Q ₂	Q ₃	LFSR output
0	011011011	0	0	0	0	
1-3	...					
4	01101	1	0	1	1	
5	0110	0	1	0	0	1
6	011	0	0	1	0	01
7	01	1	0	0	1	001
8	0	0	1	0	1	1001
9		1	0	1	1	11001



signature


not used

Quiz

**Q: Suppose CUT output is '001001'. (right bit first)
What is the signature after 6 cycles?**

ANS:

LFSR Input
(from CUT)
001001

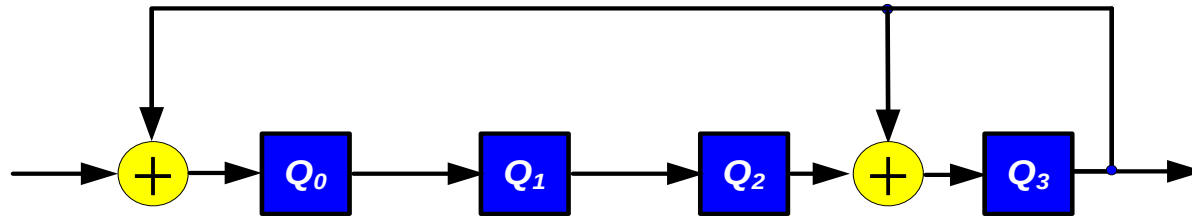

cycle	LFSR input	Q ₀	Q ₁	Q ₂	Q ₃	LFSR output
0	001001	0	0	0	0	
1-3	...					
4						
5						
6						

Too Slow. Any Better Method?

Cyclic Redundancy Code (CRC) Theory

- Represent bit streams **by polynomials**

- ♦ x is **dummy variable**
- ♦ Exponent represents **delay**
- ♦ bits are **coefficients**

$$M(x) = \sum_i b_i x^i$$

- Example: 011011011  $\rightarrow x + x^2 + x^4 + x^5 + x^7 + x^8$
 - ♦ **Left bits = LSB**, **right bits = MSB**

For more details, see reference book (BA)
or textbooks in *finite field*



Évariste Galois
1811-1832

Modular-2 Arithmetic

- **Modulo-2:** Addition (=subtraction) is XOR, Multiplication is AND
 - ♦ $0+0=0, 0+1=1, 1+0=1, 1+1=0$
 - ♦ $0 \times 0=0, 0 \times 1=0, 1 \times 0=0, 1 \times 1=1$
 - ♦ **aka. Galois Field 2, GF(2)**
- GF(2) Multiplication

GF(2) Division 

$ \begin{array}{r} (x^3 + x^2 + x + 1) \times (x^2 + x + 1) \\ \\ \begin{array}{r} x^3 + x^2 + x + 1 \\ \quad \underline{x^2 + x + 1} \\ x^3 + x^2 + x + 1 \\ \quad \underline{x^4 + x^3 + x^2 + x} \\ x^5 + x^4 + x^3 + x^2 \\ \quad \underline{x^5 + 0 + x^3 + x^2 + 0 + 1} \end{array} \end{array} $	$ \begin{array}{r} \overline{x^3 + x^2 + x + 1} \\ x^2 + x^1 + 1 \bigg) x^5 + 0 + x^3 + x^2 + 0 + 1 \\ \underline{x^5 + x^4 + x^3} \\ x^4 + 0 + x^2 \\ \underline{x^4 + x^3 + x^2} \\ x^3 + 0 + 0 \\ \underline{x^3 + x^2 + x} \\ x^2 + x + 1 \\ \underline{x^2 + x + 1} \\ 0 \end{array} $
--	--


Congruent

- $M(x) \div f(x) = Q(x) \dots R(x)$
- If $M_1(x)$ and $M_2(x)$ have **same remainders** when divided by $f(x)$
 - ♦ $M_1(x)$ and $M_2(x)$ are **congruent**
 - ♦ $M_1(x) \equiv M_2(x) \pmod{f(x)}$
- If $M(x) \equiv 0 \pmod{f(x)}$
 - ♦ $M(x)$ is **divisible** by $f(x)$

$$\begin{array}{r}
 x^3 + x^2 + x + 1 \\
 x^2 + x^1 + 1 x^5 + 0 + x^3 + x^2 + 0 + 1 \\
 \underline{x^5 + x^4 + x^3} \\
 x^4 + 0 + x^2 \\
 \underline{x^4 + x^3 + x^2} \\
 x^3 + 0 + 0 \\
 \underline{x^3 + x^2 + x} \\
 x^2 + x + 1 \\
 \underline{x^2 + x + 1} \\
 0
 \end{array}$$

$$\text{Congruent } M_1(x) \equiv M_2(x)$$


LFSR is GF(2) Divider

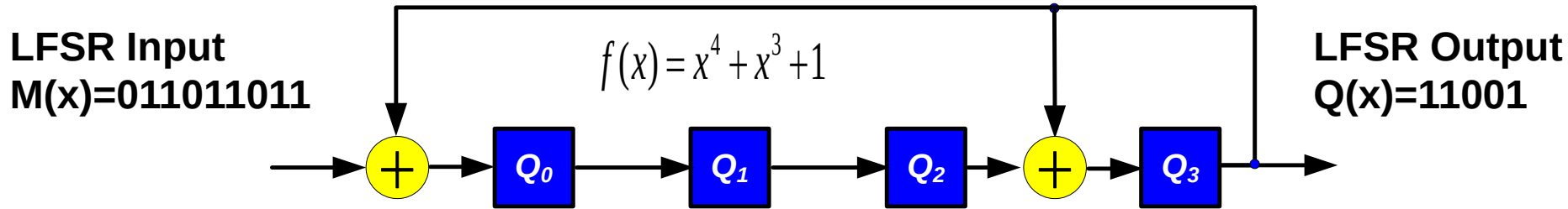

- Assume initial LFSR content = 0000, then
- $M(x) \div f(x) = Q(x) \dots R(x)$
 - ♦ LFSR Input bit stream = dividend $M(x)$
 - ♦ LFSR characteristic polynomial = divisor $f(x)$
 - ♦ LFSR output bit stream = quotient $Q(x)$
 - ♦ **Signature = Remainder** $R(x)$ 
 - ♦ $R(x) \equiv M(x) \pmod{f(x)}$

GF(2) Divider is Simple

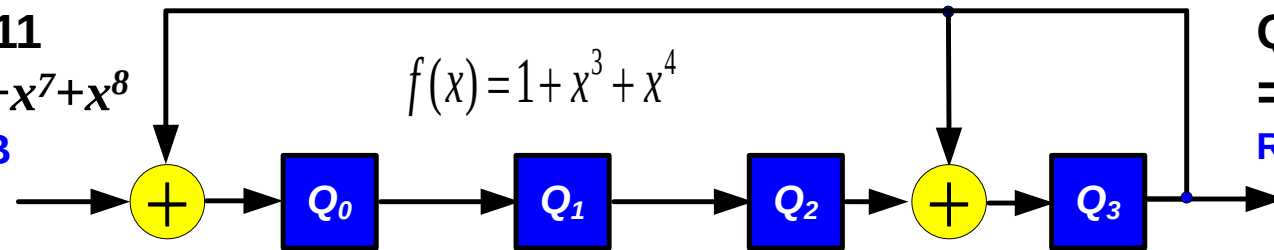$M(x)=011011011$
 $= x+x^2+x^4+x^5+x^7+x^8$
 Right bit is MSB



$Q(x)=11001$
 $= 1+x+x^4$
 Right bit is MSB

cycle	LFSR input	Q_0	Q_1	Q_2	Q_3	LFSR output
0	011011011	0	0	0	0	
1-3	...					
4	01101	1	0	1	1	
5	0110	0	1	0	0	1
6	011	0	0	1	0	01
7	01	1	0	0	1	001
8	0	0	1	0	1	1001
9		1	0	1	1	11001

remainder= $R(x)=1+x^2+x^3$

quotient= $Q(x)=1+x+x^4$


$$(x+x^2+x^4+x^5+x^7+x^8) \div (1+x^3+x^4) = 1+x+x^4 \dots 1+x^2+x^3$$

$$M(x) \div f(x) = Q(x) \dots R(x)$$

Quiz

Q: Suppose CUT output is '001001'. (right bit first)
Use GF(2) division to find quotient and remainder
ANS:

LFSR Input
(from CUT)
001001

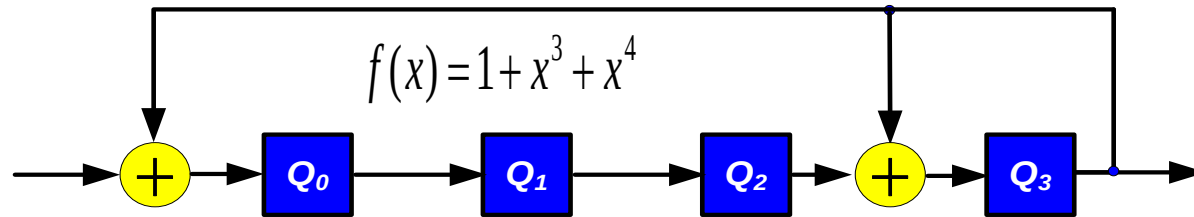

cycle	LFSR input	Q_0	Q_1	Q_2	Q_3	LFSR output
0	001001	0	0	0	0	
1-3	...					
4	00	1	0	0	1	
5	0	1	1	0	1	1
6		1	1	1	1	11


Why LFSR = Divider?

- Modular-form (Type-2) LFSR

♦ shift-and-add = shift-and-subtract = mod $f(x)$ divider

$$M(x)=011011011$$

$$= x+x^2+x^4+x^5+x^7+x^8$$

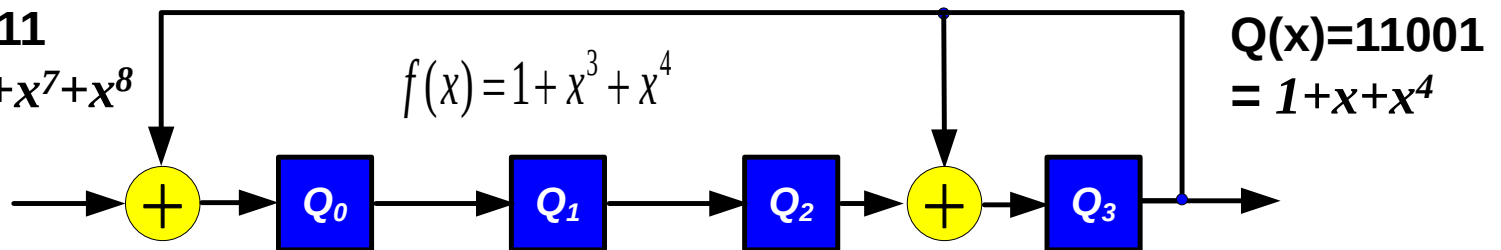


$$\begin{array}{r}
 x^4 \\
 1+x^3+x^4 \overline{) x+x^2+x^4+x^5+x^7+x^8} \\
 \underline{ x^4 } \\
 x+x^2++x^5 \\
 \dots
 \end{array}$$

cycle	LFSR input	Q ₀	Q ₁	Q ₂	Q ₃	LFSR output
0	011011011	0	0	0	0	
1-3	...					
4	01101	1	0	1	1	
5	0110	0	1	0	0	1

So We Call It “Modular-form” LFSR

How about Standard-form LFSR?

LFSR Input
011011011
Right bit first

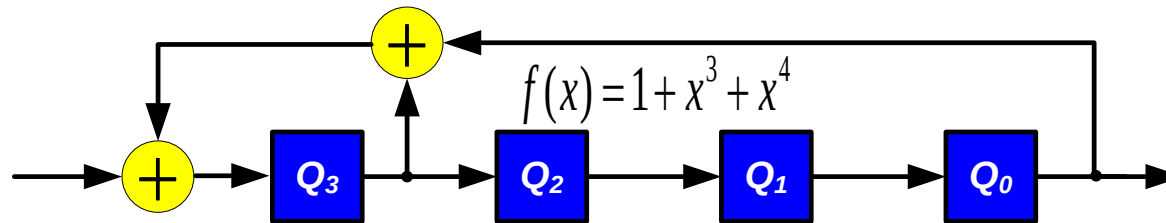

LFSR Output
11001
Right bit first

cycle	LFSR input	Q ₃	Q ₂	Q ₁	Q ₀	LFSR output
0	011011011	0	0	0	0	
1-3	...					
4	01101	1	0	0	1	
5	0110	1	1	0	0	1
6	011	1	1	1	0	01
7	01	0	1	1	1	001
8	0	0	0	1	1	1001
9		1	0	0	1	11001

**Std-form
LFSR ≠
Divider**

1 +x³ 1+x+x⁴
signature≠remainder quotient is correct

BIST Part 2

- Output Response Analysis

- ◆ Simple ORA

- ◆ LFSR-based ORA

- * Serial : compress one bit at a time

- CRC Theory

- PAL analysis


- How to design LFSR as ORA?

- * Parallel : compress multiple bits at a time

- BIST Architecture

- Issues with BIST

- Conclusions

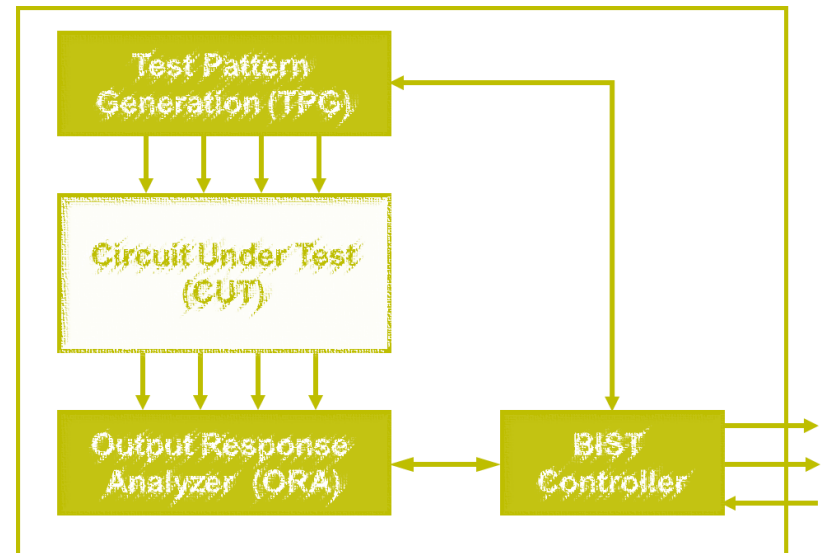

Linearity of Signature

- $[M_1(x) + M_2(x)] \bmod f(x) \equiv [M_1(x) \bmod f(x)] + [M_2(x) \bmod f(x)] \bmod f(x)$

- Example:

- ♦ $M_3(x) = M_1(x) + M_2(x)$


- * $x + x^4 + x^7 + x^8 = (x + x^2 + x^4 + x^5 + x^7 + x^8) + (x^2 + x^5)$

- ♦ Then signature $R_3(x) = R_2(x) + R_1(x)$

- * $(x + x^2 + x^4 + x^5 + x^7 + x^8) \div (1 + x^3 + x^4) = 1 + x + x^4 \dots\dots 1 + x^2 + x^3$

- * $(x^2 + x^5) \div (1 + x^3 + x^4) = 1 + x \dots\dots 1 + x + x^2 + x^3$

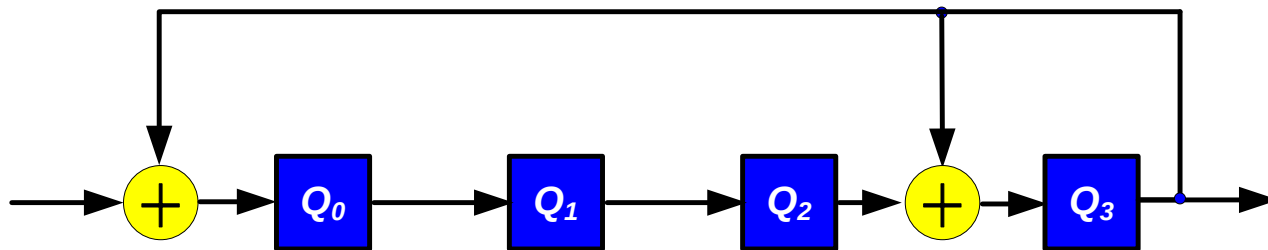- * $(x + x^4 + x^7 + x^8) \div (1 + x^3 + x^4) = x^4 \dots\dots x$



Signature of (Σ inputs) $\equiv \Sigma$ (signature of inputs)

What Is Aliasing?

- $M_{\text{good}}(x)$ is good output, $R_{\text{good}}(x)$ is gold signature
- $M_{\text{faulty}}(x)$ is faulty output, $R_{\text{faulty}}(x)$ is faulty signature
- Aliasing occurs when $R_{\text{good}}(x) = R_{\text{faulty}}(x)$

- Example:

- ♦ $M_{\text{good}}(x)$, gold signature = $1+x^2+x^3$

- * $(x+x^2+x^4+x^5+x^7+x^8) \div (1+x^3+x^4) = 1+x+x^4 \dots\dots 1+x^2+x^3$

- ♦ $M_{\text{faulty}}(x)$, faulty signature = x **no aliasing**

- * $(x + x^4 + x^7 + x^8) \div (1+x^3+x^4) = x^4 \dots\dots x$

- ♦ $M_{\text{faulty2}}(x)$, faulty signature = $1+x^2+x^3$ **aliasing!**

- * $(x^2 + x^7 + x^8) \div (1+x^3+x^4) = 1+x^4 \dots\dots 1+x^2+x^3$

Aliasing Means $R_{\text{faulty}} = R_{\text{good}}$

Aliasing Condition

- $M_{\text{good}}(x)$ is good output
- $M_{\text{faulty}}(x)$ is faulty output
- $M_{\text{error}}(x)$ = difference between $M_{\text{faulty}}(x)$ and $M_{\text{good}}(x)$

- ♦ $M_{\text{faulty}}(x) = M_{\text{good}}(x) + M_{\text{error}}(x)$

- Aliasing means

- ♦ $R_{\text{faulty}}(x) = R_{\text{good}}(x)$
 - ♦ $M_{\text{faulty}}(x) \equiv M_{\text{good}}(x) \pmod{f(x)}$

$[M1(x) + M2(x)] \pmod{f(x)} = [M1(x) \pmod{f(x)} + M2(x) \pmod{f(x)}] \pmod{f(x)}$ Assu

$M1(x)$ and $M2(x)$ are congruent $\Leftrightarrow M1(x) \equiv M2(x) \pmod{f(x)} \Leftrightarrow$ Their remainders are the same.

- Aliasing condition:

- ♦ $M_{\text{good}}(x) + M_{\text{error}}(x) \equiv M_{\text{good}}(x) \pmod{f(x)}$
 - ♦ $M_{\text{error}}(x) \equiv 0 \pmod{f(x)}$
 - ♦ i.e. $M_{\text{error}}(x)$ divisible by $f(x)$ of LFSR

Aliasing when M_{error} Divisible by f

Quiz

$M_{\text{good}}(x)$, gold signature = $1+x^2+x^3$

♦ $(x+x^2+x^4+x^5+x^7+x^8) \div (1+x^3+x^4) = 1+x+x^4 \dots\dots 1+x^2+x^3$

$M_{\text{faulty2}}(x)$, faulty signature = $1+x^2+x^3$ aliasing!

♦ $(x^2 + x^7+x^8) \div (1+x^3+x^4) = 1+x^4 \dots\dots 1+x^2+x^3$

Q1: $M_{\text{error}}(x) = ?$

ANS:

Q2: Use long division to verify that $M_{\text{error}}(x) \equiv 0 \pmod{f(x)}$

ANS:

PAL Estimate

- Assume $M(x)$, length m
 - $M_{\text{faulty}}(x) = M_{\text{good}}(x) + M_{\text{error}}(x)$
 - Divisor $f(x)$, degree N
 - Every bit has **equal probability** to flip 
 - * Every bit of $M_{\text{error}}(x)$ can be 1 with equal probability
- Total number of errors that can occur
 - = total number of nonzero $M_{\text{error}}(x)$ polynomials
 - = $2^m - 1$
- Number of errors that cause aliasing
 - = number of nonzero $M_{\text{error}}(x)$ that are divisible by $f(x)$
 - = $2^{m-N} - 1$ 

$$\begin{array}{r}
 11101 \\
 \oplus 00010 \\
 \hline
 11111
 \end{array}
 \quad m=5$$

$$PAL = \frac{2^{m-N} - 1}{2^m - 1} \approx 2^{-N} \quad (\text{if } m \gg N)$$

- 5-degree LFSR PAL=1/32; 6-degree LFSR PAL=1/64
 - LFSR increases **1 bit**, PAL decreases **50%**

BIST Part 2

- Output Response Analysis

- ◆ Simple ORA

- ◆ LFSR-based ORA

- * Serial : compress one bit at a time

- CRC Theory

- PAL analysis


- How to design LFSR as ORA?

- * Parallel : compress multiple bits at a time

- BIST Architecture

- Issues with BIST

- Conclusions

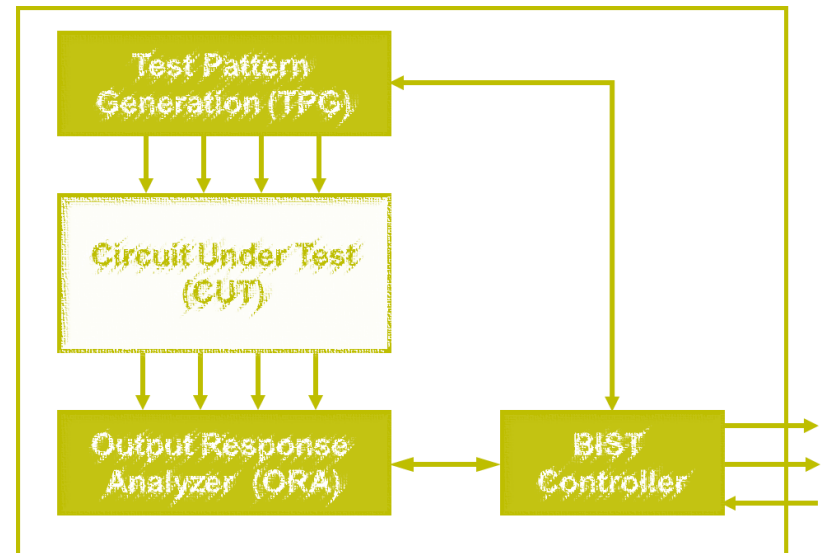

Design Guideline

- Given a PAL, design an LFSR

- ◆ 1. How many stages, $N = ?$ (Degrees of LFSR)

- * $N = -\log_2 \text{PAL}$

- ◆ 2. Which polynomial?

- * Primitive polynomial

$$\text{PAL} = \frac{2^{m-N} - 1}{2^m - 1} \approx 2^{-N} \text{ (if } m \gg N \text{)}$$

- ◆ 3. Test length, m must be greater than N

- Example: target PAL = 10^{-6} , test length = 1,000

- ◆ $N = 20$

- ◆ $\text{PAL} = 2^{-20} \approx 10^{-6}$

- ◆ Find a primitive polynomial of degree 20

- * e.g. $1 + x^3 + x^{20}$

- ◆ Test length $\gg 20$

- * Assumption valid

What Polynomial?

- Study shows [Williams 88]
 - ♦ PAL of primitive polynomial converge to final steady state value
 - * Faster than non-primitive polynomials
 - ♦ So it is good to use **primitive polynomials**

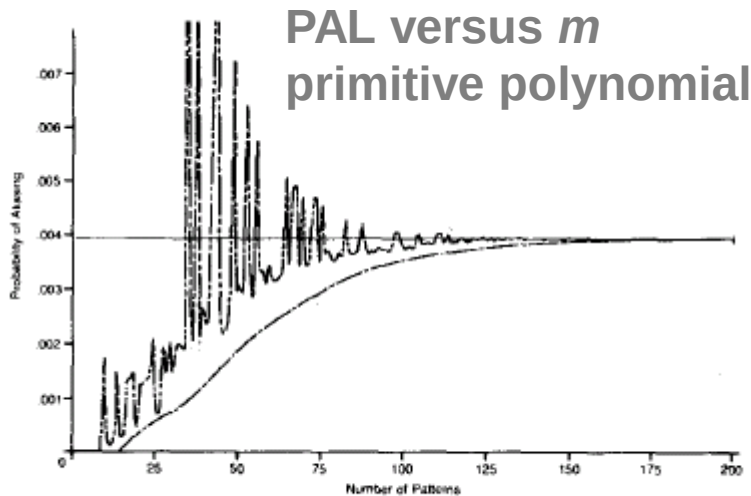


Fig. 15. Aliasing probability as a function of the test length.

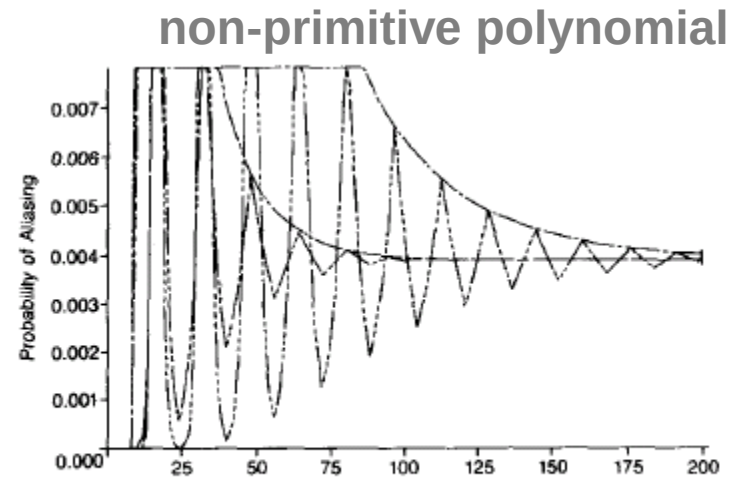


Fig. 16. Aliasing probability as a function of the test length $X^8 + 1$.

Use Primitive Polynomial

Summary

- LFSR-based ORA
 - ◆ Type-2 (modular form) LFSR is **divider**
 - ◆ Aliasing occurs when M_{error} is **divisible by f**
 - ◆ $PAL_{LFSR} = 2^{-N}$ very low
 - ◆ Use **primitive polynomial**

