




VLSI Testing

積體電路測試

Fault Collapsing

Professor James Chien-Mo James Li 李建模
Lab. of Dependable Systems (LaDS)
Graduate Institute of Electronics Engineering
National Taiwan University

Course Roadmap (EDA Topics)

 

Why Am I Learning This?

- Fault collapsing reduce number of faults
 - ◆ Speed up fault simulation and ATPG
 - ◆ Reduce Test Patterns

***“Simplicity is the ultimate sophistication.”
(Leonardo da Vinci)***

Fault Collapsing


- Introduction
- Equivalence Fault Collapsing
 - ◆ Fanout-free circuits
 - ◆ Circuits with fanout
- Dominance Fault Collapsing
 - ◆ Fanout-free circuits
 - ◆ Circuits with fanout
- Discussions
- Conclusion

Introduction

- **Why Fault Collapsing?**
 - ◆ Reduce number of faults so that
 - * Speed up ATPG
 - * Shorten test set
- **How?**
 - ◆ Quickly find *representative faults*
 - ◆ Use only those representative faults for ATPG
- **Requirement of fault collapsing algorithm**
 - ◆ Must be fast; otherwise, it is not worth doing
- **There are many different ways to do fault collapsing**
 - ◆ Obtaining the *minimum* solution is not so important
 - ◆ As long as we do not miss any fault

Equivalent Faults

 - Faults f and g are *functionally equivalent* (or simply *equivalent*)
 - if faulty outputs of them are identical for *all* test patterns
- Example: $A/0$ $B/0$ and $C/0$ are all **equivalent faults**
 - They belong to the same *equivalent fault class*



Input		Output						
A	B	good	$A/0$	$C/0$	$B/0$	$A/1$	$C/1$	$B/1$
0	0	0	0	0	0	0	<u>1</u>	0
0	1	0	0	0	0	<u>1</u>	<u>1</u>	0
1	0	0	0	0	0	0	<u>1</u>	<u>1</u>
1	1	1	<u>0</u>	<u>0</u>	<u>0</u>	1	1	1


Properties of Equivalence

- Equivalence relationship is **symmetric**

- if fault f is equivalent to fault g , then fault g is equivalent to fault f

- Equivalence relationship is also **transitive**

 - if fault f is equivalent to fault g and fault g is equivalent to fault h , then fault f is equivalent to fault h




- Example

- $A/0$ fault is equivalent to $B/0$ fault, which is also equivalent to $C/0$ fault. These three faults belong to the same **equivalence class**

Input		Output						
A	B	good	A/0	C/0	B/0	A/1	C/1	B/1
0	0	0	0	0	0	0	<u>1</u>	0
0	1	0	0	0	0	<u>1</u>	<u>1</u>	0
1	0	0	0	0	0	0	<u>1</u>	<u>1</u>
1	1	1	<u>0</u>	<u>0</u>	<u>0</u>	1	1	1

Equivalence Fault Collapsing, EFC

 - EFC reduces fault list using fault equivalence relationship
 - ♦ Select **one representative fault** from every equivalent class
- Example:
 - ♦ Originally six faults per 2-input gate
 - ♦ After EFC, only four faults per gate
 - ♦ **6→4**



- NOTE: EFC is not unique
 - ♦ {A/0, A/1, B/1, C/1} is also EFC for AND gate

How to Perform EFC?

- EFC can be performed by *functional analysis* or *structure analysis*
- **Functional analysis**
 - ♦ Apply **all possible** test patterns and fault simulate two faults
 - * If same faulty outputs , two faults are equivalent
 - ♦ Exhaustive functional time consuming
 - * 2^n test patterns may be needed for an n -input circuit
- **Structure analysis**
 - ♦ Identify equivalent faults by circuit structure
 - ♦ No test patterns applied
- **Many different structure analysis approaches**
 - ♦ In this lecture, we show a linear time structure analysis example
 - ♦ Resulting equivalence collapsed fault list may not be minimal
 - * but good enough for most applications

Structure Analysis Is Enough for Most Applications

EFC on Fanout-free Circuits


- **Our EFC Rules**

and fanout stem

- ♦ (1) both stuck-at one and zero faults **for every primary output**
- ♦ (2) one collapsed fault **for each gate input**
 - * stuck-at **non-controlling values** (see slide 8)

 
- **Example**

- ♦ keep both H/0 and H/1 faults for primary output H
- ♦ keep one fault for each gate input,
 - * A/0 and B/0 for OR gate G₁ and etc
- ♦ Original **14** faults → **8** faults after EFC
- ♦ Why faults on the gate outputs are removed?
 - * gate G₁ output stuck-at zero fault is equivalent to C/0 fault, which is equivalent to E/1, which is equivalent to H/0.



EFC on Circuits with Fanouts

 - Fanout stem faults are NOT always equivalent to fanout branch faults
- Example:
 - ♦ E/0 is equivalent to F/0
 - * but not equivalent to L/0
 - ♦ No two faults are equivalent



*This functional analysis is slow

Input			Output						
A	B	C	good	E/0	F/0	L/0	E/1	F/1	L/1
0	0	0	0	0	0	0	<u>1</u>	<u>1</u>	0
0	0	1	1	<u>0</u>	<u>0</u>	1	1	1	1
0	1	0	1	<u>0</u>	<u>0</u>	1	1	1	1
0	1	1	1	<u>0</u>	<u>0</u>	1	1	1	1
1	0	0	0	0	0	0	0	<u>1</u>	0
1	0	1	0	0	0	<u>1</u>	0	0	0
1	1	0	0	0	0	<u>1</u>	0	0	0
1	1	1	0	0	0	<u>1</u>	0	0	0


How to Handle Circuits w/ Fanouts?

- **Stem analysis** determines equivalent faults on fanout stem and its branches
 - ◆ However, stem analysis is time consuming
 - * not worth the time
 - * details skipped in this lecture
- An approximate solution
 - ◆ Partition circuit into independent *fanout-free subcircuits*
 - ◆ Every fanout stem treated as a primary output
 - * both $s@1$ $s@0$ faults are included on branches
 - * They are *NOT* collapsed

Treat each FFS partition independently

 Example

- 2 partitions
- Originally 18 faults, → after EFC 10 faults



- NOTE:
 - ♦ Inverter G_3 ignored
 - ♦ because its input fault $s@0$ is always equivalent to its output $s@1$ fault

Simple_EFC Algorithm


- **Linear time** (NOT unique; other EFC algorithm is possible)

```
Simple_EFC (N) /*N is a netlist*/
0. fault_list = {};
1. foreach gate or PO or PI  $g$  in  $N$ 
2.   if ((  $g$  is PO) || ( $g$  is PI and fanout stem)) then
3.     fault_list = fault_list  $\cup$   $g$  stuck-at 0 and stuck-at 1;
4.   else if (output of gate  $g$  is fanout stem) then
5.     fault_list = fault_list  $\cup$   $g$  output stuck-at 0 and 1;
6.   end if
7.   if (gate  $g$  is AND) || (gate  $g$  is NAND) then
8.     fault_list = fault_list  $\cup$   $g$  input stuck-at 1;
9.   else if (gate  $g$  is OR) || (gate  $g$  is NOR) then
10.    fault_list = fault_list  $\cup$   $g$  input stuck-at 0;
11.   end if
12. end foreach
13. return (fault_list );
```

*This structural analysis is fast.

 Problems of *Simple_EFC* (1)


- Does **NOT** guarantee optimal result because it lacks stem analysis
 - ♦ For example, E/0 fault actually equivalent to K/0 fault
 - * but they both appear after *Simple_EFC*
 - ♦ Often acceptable in most cases



Input			Output						
A	B	C	good	E/0	F/0	L/0	E/1	F/1	L/1
0	0	0	0	0	0	0	<u>1</u>	<u>1</u>	0
0	0	1	1	<u>0</u>	<u>0</u>	1	1	1	1
0	1	0	1	<u>0</u>	<u>0</u>	1	1	1	1
0	1	1	1	<u>0</u>	<u>0</u>	1	1	1	1
1	0	0	0	0	0	0	0	<u>1</u>	0
1	0	1	0	0	0	<u>1</u>	0	0	0
1	1	0	0	0	0	<u>1</u>	0	0	0
1	1	1	0	0	0	<u>1</u>	0	0	0

 Problems of *Simple_EFC* (2)




- **Link** between original (uncollapsed) faults and their corresponding collapsed faults is **lost**
- **Example:**
 - ♦ No link between four faults {F/0, J/1, H/1, K/0} in same equivalence class and their collapsed fault K/0
- Links between uncollapsed faults and collapsed faults are needed when calculating the **uncollapsed fault coverage**
 - ♦ Example: suppose we detect A/1 K/0 and B/0 faults
 - * Collapsed fault coverage is $3/10 = 30\%$
 - * But uncollapsed fault coverage is $?/18 = ?$



FFT

- Q1: Why did we choose C/0?

♦ why not A/0 ? B/0?

   

- Q2: How do we modify the *Simple_EFC* algorithm to calculate number of faults in each equivalence class?

♦ i.e. how do we know there are 4 faults in K/0 equivalence class?

