 


Fault Collapsing


- Introduction
- Equivalence Fault Collapsing
 - ◆ Fanout-free circuits
 - ◆ Circuits with fanouts
- Dominance Fault Collapsing
 - ◆ Fanout-free circuits
 - ◆ Circuits with fanouts
- Checkpoint Theorem (1976)
- Conclusion

Fault Dominance

- **Detecting set of fault f (T_f)** = set of all test patterns that detect fault f
- **Fault f dominates fault g** if the detecting set of f contains that of g
 - ♦ $T_f \supseteq T_g$
- **Example: C/1 fault dominates A/1 fault**
 - ♦ C/1 detecting set {00, 01, 10} contains A/1 detecting set {01}
 - ♦ C/1 is **dominating fault**; A/1 is **dominated fault**



Input		Output						
A	B	good	A/0	C/0	B/0	A/1	C/1	B/1
0	0	0	0	0	0	0	<u>1</u>	0
0	1	0	0	0	0	<u>1</u>	<u>1</u>	0
1	0	0	0	0	0	0	<u>1</u>	<u>1</u>
1	1	1	<u>0</u>	<u>0</u>	<u>0</u>	1	1	1

 

Quiz

Q: Is dominance relation transitive?

if f dominates g , and g dominates h , then f dominates h ?


A:

Q: Is dominance relation symmetric?

if f dominates g , then g dominates f ?

A:

 
$f \leftrightarrow g$: equivalence
 $f \rightarrow g$: dominance



Dominance Fault Collapsing, DFC

- DFC reduces fault list using fault dominance relation
 - ♦ If a test pattern detects a *dominated fault*, then it must detect its *dominating fault*. So **dominating faults can be removed** for ATPG
- Example:
 - ♦ **C/1** fault can be removed. Similarly, **A/0**, **B/0** also removed
 - ♦ Minimum {A/1, B/1, C/0} 3 faults remains after DFC


Input		Output						
A	B	Good	A/0	C/0	B/0	A/1	C/1	B/1
0	0	0	0	0	0	0	<u>1</u>	0
0	1	0	0	0	0	<u>1</u>	<u>1</u>	0
1	0	0	0	0	0	0	<u>1</u>	<u>1</u>
1	1	1	<u>0</u>	<u>0</u>	<u>0</u>	1	1	1

 


Minimum 3 faults after DFC

DFC on Elementary Gates

 - 2-input AND/OR/NAND/NOR elementary gates
 - ♦ Originally 6 faults $\rightarrow$ 4 faults after EFC $\rightarrow$ 3 faults after DFC
- For n -input elementary gate,
 - ♦ $n+1$ stuck-at faults after DFC





DFC on Fanout-free Circuits

 


blue SA0
red SA1

push to PI

  

all-PI gates reduce further

 

- Two observations:

- ① All gate input faults removed; except primary inputs

- ② All gate output faults removed; except all-PI gates

- This is also applicable to other elementary gates. Why? FFT

DFC Rules for Fanout-free Circuits


DFC Rules

fanout branches = PIs

fanout stems = POs


- (1) **one** DFC collapsed fault for **every primary input**
- (2) **one** DFC collapsed fault for each **all-PI gate output***

*all-PI gate = gate inputs are all PI

 





 
• Example

- ♦ Original **14** faults → **8** faults after EFC → **5** faults after DFC



Quiz

     Q: Please perform DFC on this fanout-free circuit. (Please label their stuck- values)




Fault Collapsing

- Introduction
- Equivalence Fault Collapsing
 - ◆ Fanout-free circuits
 - ◆ Fanout
- **Dominance Fault Collapsing**
 - ◆ Fanout-free circuits
 - ◆ Circuits with fanout
- Checkpoint Theorem
- Conclusion

Fanout Stem and Branches

- Fanout branch faults do NOT always dominate fanout stem faults
- Example: $F/1$ fault dominates $E/1$. but $L/1$ fault does not dominate $E/1$
- Stem analysis* of fanout faults is time consuming


Input			Output						
A	B	C	good	E/0	F/0	L/0	E/1	F/1	L/1
0	0	0	0	0	0	0	<u>1</u>	<u>1</u>	0
0	0	1	1	<u>0</u>	<u>0</u>	1	1	1	1
0	1	0	1	<u>0</u>	<u>0</u>	1	1	1	1
0	1	1	1	<u>0</u>	<u>0</u>	1	1	1	1
1	0	0	0	0	0	0	0	<u>1</u>	0
1	0	1	0	0	0	<u>1</u>	0	0	0
1	1	0	0	0	0	<u>1</u>	0	0	0
1	1	1	0	0	0	<u>1</u>	0	0	0

 

Hard to Analyze Dominance between Stem and Branches


How to Handle Circuits w/ Fanouts?

 - Approximate solution: **Partition** circuit into fanout-free subcircuits
 - ♦ DFC each subcircuit **independently**
- Example:
 - ♦ J is consider input because inverter G_3 is ignored
 - ♦ Original **18** faults, $\rightarrow$ after EFC **10** faults $\rightarrow$ after DFC **7** faults
 - ♦ NOTE: this solution is **NOT optimal**
 - * $J/0$ is equivalent to $F/1$, which dominates $E/1$



Simple_DFC Algorithm

 - **Linear time**
- **Does NOT guarantee minimum DFC**
 - ♦ **No stem analysis**




```

Simple_DFC (N) /*N is a netlist*/
0. fault_list = {};
1. foreach gate or PI or PO  $g$  in  $N$ 
2.   if (( $g$  is PI and fanout stem) || ( $g$  is PO and fanout branch)) then
3.     fault_list = fault_list  $\cup$   $g$  output stuck-at 0 and 1;
4.   else if ( $g$  is gate) then
5.     foreach gate input  $i$  of gate  $g$ 
6.        $h$  = backtrack inverters starting from  $i$ ;
7.       if ( $h$  is PI or fanout branch) then /* rule #1 */
8.         if (gate  $g$  is AND) || (gate  $g$  is NAND) then
9.           fault_list = fault_list  $\cup$   $i$  stuck-at 1;
10.        else if (gate  $g$  is OR) || (gate  $g$  is NOR)
11.          fault_list = fault_list  $\cup$   $i$  stuck-at 0;
12.        end if
13.      end if
14.    end foreach
15.    if (every gate input of  $g$  has a fault) then /* rule #2 */
16.      if (gate  $g$  is AND) || (gate  $g$  is NOR) then
17.        fault_list = fault_list  $\cup$   $g$  output stuck-at 0;
18.      else if (gate  $g$  is OR) || (gate  $g$  is NAND) then
19.        fault_list = fault_list  $\cup$   $g$  output stuck-at 1;
20.      end if
21.    end if
22.  end if
23. end foreach
24. return (fault_list);
    
```

Quiz

 **Q: Please perform DFC on this circuit.
(Please label their stuck- values)**



```

Simple_DFC (N) /*N is a netlist*/
0. fault_list = {};
1. foreach gate or PI or PO g in N
2.   if ((g is PI and fanout stem) || (g is PO and fanout branch)) then
3.     fault_list = fault_list ∪ g output stuck-at 0 and 1;
4.   else if (g is gate) then
5.     foreach gate input i of gate g
6.       h = backtrace inverters starting from i;
7.       if (h is PI or fanout branch) then /* rule #1 */
8.         if (gate g is AND) || (gate g is NAND) then
9.           fault_list = fault_list ∪ i stuck-at 1;
10.        else if (gate g is OR) || (gate g is NOR)
11.          fault_list = fault_list ∪ i stuck-at 0;
12.        end if
13.      end if
14.    end foreach
15.    if (every gate input of g has a fault) then /* rule #2 */
16.      if (gate g is AND) || (gate g is NOR) then
17.        fault_list = fault_list ∪ g output stuck-at 0;
18.      else if (gate g is OR) || (gate g is NAND) then
19.        fault_list = fault_list ∪ g output stuck-at 1;
20.      end if
21.    end if
22.  end if
23. end foreach
24. return (fault_list );
    
```


Fault Collapsing

- Introduction
- Equivalence Fault Collapsing
 - ◆ Fanout-free circuits
 - ◆ Fanout
- Dominance Fault Collapsing
 - ◆ Fanout-free circuits
 - ◆ Circuits with fanout
- Checkpoint Theorem
- Conclusion

Checkpoint Theorem [Breuer 76]

If a test detects all SSF on all checkpoints, this test detects all SSF in the circuit.

 
- Checkpoints = primary inputs + fanout branches
- Example:
 - ♦ 10 faults on checkpoints
 - ♦ Originally 18 faults, after EFC 10 faults, after DFC 7 faults




$$|\text{CHKPT}| \geq |\text{EFC}| \geq |\text{DFC}|$$

Proof

 - Partition circuit into fanout-free subcircuits
- Use dominance relationship to remove faults from right to left until
 - ♦ (1) PI
 - ♦ (2) Fanout branch



 *can be changed to other elementary gates



Chkpt are Simple Alternative to EFC/DFC

Fault Collapsing

- Introduction
- Equivalence Fault Collapsing
 - ◆ Fanout-free circuits
 - ◆ Fanout
- Dominance Fault Collapsing
 - ◆ Fanout-free circuits
 - ◆ Circuits with fanout
- Checkpoint Theorem
- **Conclusion**

Example ATPG Report

	uncollapsed	Collapsed (typically EFC)
Total Faults	1,234	800
Detected faults	1,000	700
Untestable faults	230	98
Aborted faults	4	2
Fault Coverage	1,000/1,234	700/800

CollapseRatio

$$= \frac{\text{number of } \textit{collapsed} \text{ faults}}{\text{number of } \textit{uncollapsed} \text{ faults}} \times 100\%$$

$$= \frac{800}{1234} \approx 64.8\%$$

uncollapsed F.C.

$$= \frac{\text{detected } \textit{uncollapsed} \text{ faults}}{\text{total } \textit{uncollapsed} \text{ faults}} \times 100\%$$


Collapsed F.C.

$$= \frac{\text{detected } \textit{collapsed} \text{ faults}}{\text{total } \textit{collapsed} \text{ faults}} \times 100\%$$

Why DFC not Used in Practice?

- Because DFC fault coverage is *pessimistic*. A test pattern can detect a dominating fault without detecting its dominated fault
- Example: ABC=100 does *NOT* detect dominated fault **E/1**, but it detects dominating fault **F/1**
 - since F/1 is removed, this is not counted in DFC coverage

Input			Output						
A	B	C	good	E/0	F/0	L/0	E/1	F/1	L/1
0	0	0	0	0	0	0	1	1	0
0	0	1	1	0	0	1	1	1	1
0	1	0	1	0	0	1	1	1	1
0	1	1	1	0	0	1	1	1	1
1	0	0	0	0	0	0	0	<u>1</u>	0
1	0	1	0	0	0	1	0	0	0
1	1	0	0	0	0	1	0	0	0
1	1	1	0	0	0	1	0	0	0

 


Conclusions

- Fault collapsing reduces size of fault list
 - ◆ Speed up ATPG, Shorten test length
- DFC Rules:
 - ◆ (1) one fault on PI (2) one fault on output of all-PI gate
- DFC is more aggressive than EFC
 - ◆ but DFC not often used because its FC is pessimistic
- Checkpoint Theorem:
 - ◆ Detecting all checkpoint faults is good enough
 - ◆ Checkpoints are (1) PI, (2) fanout branches

FFT

 - Q1: We only show DFC rule on AND gate fanout-free circuits.
 - ♦ Does it also applicable to other elementary gates? Please show why the other faults can be reduced



- Q2: Can we DFC on XOR gate? How about EFC?

References

- **[Breuer 76] M. A. Breuer and A. D. Friedman, Diagnosis & Reliable Design of Digital Systems. Woodland Hills, CA: Computer Science Press, 1976.**